

# ECE154A — Discussion 00

---

George Higgins Hutchinson


October 8, 2021

# ECE154A — Discussion 00

---

George Higgins Hutchinson


October 8, 2021

 

## Keep your eyes open for...

- PSet 1: due ~~Wednesday, Oct 6~~ Monday, Oct 11
- Lab 2: should be officially assigned soon

# Array Multiplier — Practice Problem


 


1 AND  
 $5 \rightarrow \text{Count}$   
 $3+5$

Let  $t_{AND} = 2\text{ps}$ ,  $t_{XOR} = 4\text{ps}$ ,  $t_{OR} = 1\text{ps}$ .

What is the critical path delay?  $2\text{ps} + 5 \cdot 7\text{ps} + 3 \cdot 8\text{ps} = 61\text{ps}$


# Carry-Select Adder

  
 
# Carry-Select Adder

- Write a logic expression for the 2:1 muxes.

$$out = a \cdot sel + \overline{sel} \cdot b$$



- Write boolean expressions for both outputs of the full adder cells.

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + C_{in}(A \oplus B) = AB + C_{in}A + C_{in}B$$

- Identify the critical path, and calculate the delay (assume path-invariant full adder)
- Derive general expressions for area and delay in an N-bit carry-select adder, split into k blocks.

# Carry-Select Adder

- Write a logic expression for the 2:1 muxes.  
$$Out = !Sel * a + Sel * b$$
- Write boolean expressions for both outputs of the full adder cells.
- Identify the critical path, and calculate the delay (assume path-invariant full adder)
- Derive general expressions for area and delay in an N-bit carry-select adder, split into k blocks.



# Carry-Select Adder

- Write a logic expression for the 2:1 muxes.

$$Out = !Sel * a + Sel * b$$

- Write boolean expressions for both outputs of the full adder cells.

$$S = X \oplus B \oplus C_{in}; C_{out} = A * B + A * C_{in} + B * C_{in}$$

- Identify the critical path, and calculate the delay (assume path-invariant full adder)
- Derive general expressions for area and delay in an N-bit carry-select adder, split into k blocks.

# Carry-Select Adder

- Write a logic expression for the 2:1 muxes.

$$Out = !Sel * a + Sel * b$$

- Write boolean expressions for both outputs of the full adder cells.

$$S = X \oplus B \oplus C_{in}; C_{out} = A * B + A * C_{in} + B * C_{in}$$

- Identify the critical path, and calculate the delay (assume path-invariant full adder)

$$t = 4t_{FA} + 3t_{MUX}$$

- Derive general expressions for area and delay in an N-bit carry-select adder, split into k blocks.

$$A = (2N - k)A_{FA} + (k - 1)A_{MUX}$$
$$t = k t_{FA} + (k - 1) t_{MUX}$$

$$\begin{matrix} N \\ k \\ t_{FA}, A_{FA} \\ t_{MUX}, A_{MUX} \end{matrix}$$

# Carry-Select Adder

- Write a logic expression for the 2:1 muxes.

$$Out = !Sel * a + Sel * b$$

- Write boolean expressions for both outputs of the full adder cells.

$$S = X \oplus B \oplus C_{in}; C_{out} = A * B + A * C_{in} + B * C_{in}$$

- Identify the critical path, and calculate the delay (assume path-invariant full adder)


$$t = 4t_{FA} + 3t_{MUX}$$

- Derive general expressions for area and delay in an N-bit carry-select adder, split into *in  $k$  blocks* blocks of  $k$ .

$$A = kA_{FA} + \frac{N}{k-1}(2kA_{FA} + (k+1)A_{MUX}); t = kt_{FA} + \frac{N}{k-1}t_{MUX}$$

Wait, we can replace some of those cells with half-adders (constant  $C_{in}$ ) . . .

 - Write Boolean expressions and draw gate diagrams for half-adders with either constant carry in.
- Assume a delay of  $\frac{1}{3}t_{FA}$  along all paths of the half-adders. Without changing the core idea, suggest a change to the structure of the adder to reduce delay.



Wait, we can replace some of those cells with half-adders (constant  $C_{in}$ ). . .

- Write Boolean expressions and draw gate diagrams for half-adders with either constant carry in.
- Assume a delay of  $\frac{1}{3}t_{FA}$  along all paths of the half-adders. Without changing the core idea, suggest a change to the structure of the adder to reduce delay. Group as 5-4-4-3 instead of 4-4-4-4. Reduced initial carry chain saves a full-adder delay. Discuss: why can't we keep doing this?

# Mystery Code!

0x00000004	main:	li \$a0, 1
0x00000008		jal mystery
0x0000000c		addu \$a0, \$0, \$v0
0x00000010		jal mystery
0x00000014		addu \$a0, \$0, \$v0
0x00000018		jal mystery
0x0000001c		addu \$a0, \$0, \$v0
0x00000020		jal mystery
<hr/>		
0x80000004	mystery:	lui \$t0, 0xffff
0x80000008		lui \$t2, %Hi(mystery)
0x8000000c		ori \$t2, %Lo(mystery)
0x80000010		addiu \$t1, \$0, 0
0x80000014		andi \$a0, \$a0, 0xffff
0x80000018		add \$v0, \$a0, \$t1
0x8000001c		lw \$t3, 12(\$t2)
0x80000020		and \$t3, \$t3, \$a0
0x80000024		or \$t3, \$t3, \$a0
0x8000002c		sw \$t3, 12(\$t2)
0x80000030		jr \$ra

What does it do? After 1 run? 2? N?